

**ECE 120 Second Midterm Exam  
Fall 2017**

Tuesday, October 24, 2017

Name: SOLUTIONS

NetID: \_\_\_\_\_

Discussion Section and TA Name:

11:00 AM	<input type="checkbox"/>	AD1 Ruby	<input type="checkbox"/>	AD8 Matt
12:00 PM	<input type="checkbox"/>	AD2 David	<input type="checkbox"/>	AD9 Matt
1:00 PM	<input type="checkbox"/>	AD3 David	<input type="checkbox"/>	ADA Yu-Hsuan
2:00 PM	<input type="checkbox"/>	AD4 Wanzheng	<input type="checkbox"/>	ADB Zhaoheng
3:00 PM	<input type="checkbox"/>	AD5 Wanzheng		
4:00 PM	<input type="checkbox"/>	AD6 Spencer	<input type="checkbox"/>	ADC Ruby
5:00 PM	<input type="checkbox"/>	AD7 Spencer	<input type="checkbox"/>	ADD Zhaoheng

- Be sure that your exam booklet has 8 pages.
- Write your name and netid and check your discussion section on this page.
- Do not tear the exam booklet apart, except for the last page.
- Use backs of pages for scratch work if needed.
- This is a closed book exam. You may not use a calculator.
- You are allowed one handwritten 8.5 x 11" sheet of notes (both sides).
- Absolutely no interaction between students is allowed.
- Clearly indicate any assumptions that you make.
- The questions are not weighted equally. Budget your time accordingly.
- Show your work.

Problem 1      16 points      \_\_\_\_\_

Problem 2      17 points      \_\_\_\_\_

Problem 3      16 points      \_\_\_\_\_

Problem 4      17 points      \_\_\_\_\_

Problem 5      18 points      \_\_\_\_\_


Problem 6      16 points      \_\_\_\_\_

---

Total              100 points      \_\_\_\_\_

**Problem 1 (16 points): CMOS Gates and Truth Tables**

 1. (8 points) Fill in the truth table with 0s and 1s only for the CMOS circuit below.



A	B	C	OUT
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

2. (8 points) You will help design a circuit that converts a 3-bit two's complement number  $T_2T_1T_0$  into a 2-bit unsigned number  $U_1U_0$  with the same magnitude. For example:

$$\text{If } T_2T_1T_0=111 \text{ then } U_1U_0=01$$

Use **don't cares** if you cannot represent the magnitude as a 2-bit unsigned number. Describe your circuit as a truth table below. One row has been provided for you.

$T_2$	$T_1$	$T_0$	$U_1$	$U_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	X	X
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

**Problem 2 (17 points): Simplification with Don't Cares and 2-level Design**

1. Consider the 4-variable function  $E(A,B,C,D)$ , with the following K-map (drawn twice). **Note:** there are extra copies of this K-map on the last page of the exam. Use them for scratch work, but they will **not** be graded. Make sure to mark the two K-maps below correctly.

Minimal SOP

 $E(A,B,C,D)$ 

AB

--- alternate

		00	01	11	10
00		1	1	0	1
01		0	1	1	X
11		0	X	X	0
10		0	0	0	0

Minimal POS

 $E(A,B,C,D)$ 

AB

		00	01	11	10
00		1	1	0	1
01		0	1	1	X
11		0	X	X	0
10		0	0	0	0

- a. (6 points) Give a **minimal SOP** expression for  $E(A,B,C,D)$  and show the corresponding loops on the **left map**.

Non-unique


Minimal SOP:  $E(A,B,C,D) = \underline{BD + A'C'D' + B'C'D'}$       alternate:  $AB'C', C'BA'$

- b. (6 points) Give a **minimal POS** expression for  $E(A,B,C,D)$  and show the corresponding loops on the **right map**.

Unique

Minimal POS:  $E(A,B,C,D) = \underline{C' (A' + B' + D) (B + D')}$

 2. (5 points) The function  $G(W,X,Y,Z) = W'(Y+Z')(X+Y'+Z)$  is in minimal POS form. Draw the implementation of this function as a 2-level circuit using NOR gates only. Use as few NOR gates as possible for full credit. Assume complemented inputs are available. Clearly label all signals.




### Problem 3 (16 points): Bit-Sliced Design

Let  $A = a_{n-1} \dots a_2a_1a_0$  be an  $n$ -bit input.

Design a circuit which outputs  $z = 1$  if  $A$  contains **exactly two 1s**. For example, for  $n = 5$ :

- if  $A = 10010$ , then  $z = 1$
- if  $A = 00100$ , then  $z = 0$
- if  $A = 01111$ , then  $z = 0$

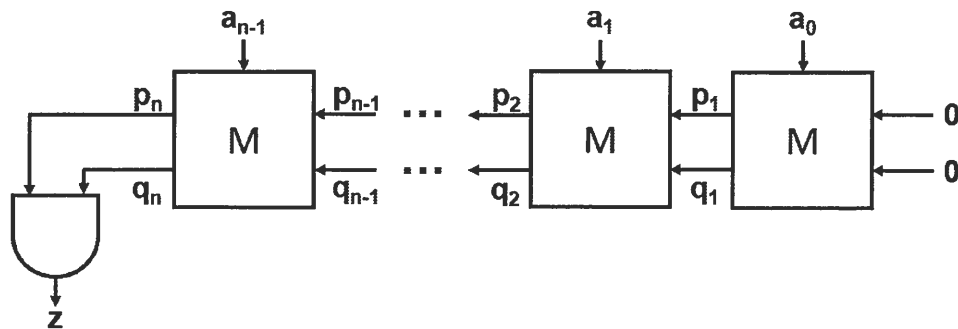Your implementation should use the bit-sliced design shown below. Each identical copy of network  $M$  has inputs  $a_i$ ,  $p_i$  and  $q_i$ , and has outputs  $p_{i+1}$  and  $q_{i+1}$ .



1. (8 points) Give meanings to each combination of the carry bits  $p_{i+1}q_{i+1}$  in the table below, so that they are **consistent with the diagram above**. One meaning has been provided to you.

$p_{i+1}$	$q_{i+1}$	Meaning
0	0	No 1s have been seen so far
0	1	Exactly one 1 has been seen so far
1	0	More than two 1s have been seen so far
1	1	Exactly two 1s have been seen so far


2. (8 points) Fill in the K-maps below for  $p_{i+1}$  and  $q_{i+1}$ .

		$p_i q_i$			
$p_{i+1}$		00	01	11	10
$a_i$	0	0	0	1	1
	1	0	1	1	1

		$p_i q_i$			
$q_{i+1}$		00	01	11	10
$a_i$	0	0	1	1	0
	1	1	1	0	0

**Problem 4 (17 points): Sequential Feedback Circuits and Decoders**

 1. (9 points) Circle all correct answers to the following questions about the circuit shown on the right. **Note:** there are extra copies of this circuit on the last page of the exam. Use them for scratch work, but they will **not** be graded.



Which inputs AB force the output C to a steady value of 0 regardless of the initial value of C?

00   01   10   11   None


Which inputs AB force the output C to a steady value of 1 regardless of the initial value of C?

00   01   10   11   None

Which inputs AB make the output C switch between 0 and 1 indefinitely?

00   01   10   11   None

 2. (8 points) Implement the Boolean function  $F = X(Y+Z)$  using the 3:8 decoder (without enable input) shown below. Label all inputs to the decoder and connect the decoder to the OR gate using **wires only**. You may not add any components nor any additional gates. Complemented inputs are **not** available.




### Problem 5 (18 points): Registers

Consider a 3-bit shift register that has the functionality specified in the table to the right.

1. (14 points) Label the inputs to the muxes to complete the design of this 3-bit register that performs the operations listed in the table. Use labels and do not draw any additional gates or wires.

A	B	Operation
0	0	Hold value
0	1	Flip all bits
1	0	Arithmetic shift right
1	1	Logical shift left

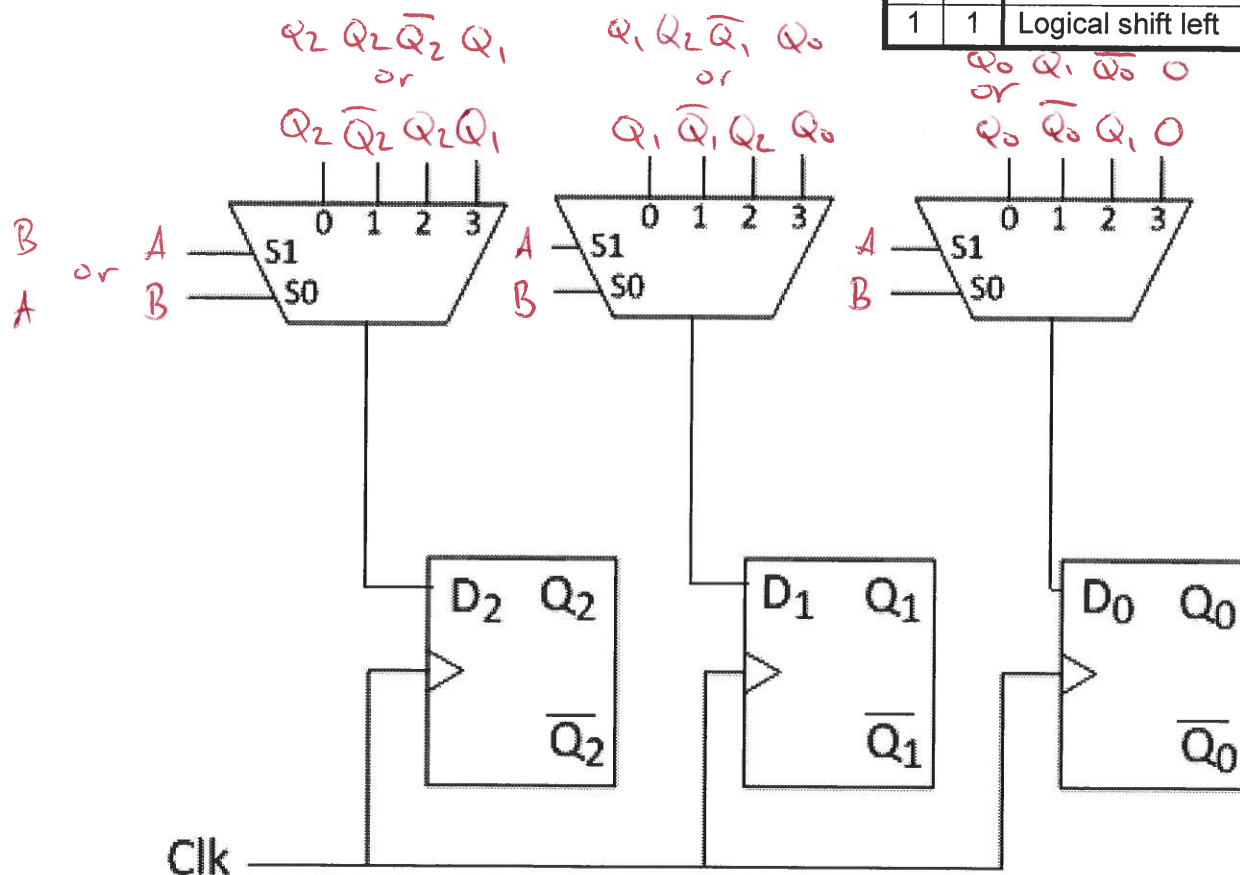

2. (2 points) If the shift register initially stores  $Q_2Q_1Q_0=101$ , what is stored in the register after one clock cycle when  $AB=10$ ?

Answer:  $Q_2Q_1Q_0=$  110

3. (2 points) If the shift register initially stores  $Q_2Q_1Q_0=000$ , and in the next clock cycle, the register has the values  $Q_2Q_1Q_0=000$ , which of the following operations could the register be implementing? Circle ALL possible answers.

Hold value

Flip all bits

Arithmetic shift right



Logical shift left

**Problem 6 (16 points): Designing Logic with Components**

Label the inputs to the muxes and the logic gate provided below to complete the design of the 4 variable function  $F$  given by the truth table to the right. If you need to refer to the outputs of the muxes or the logic gate, use the names we have specified in the diagram.

**Use labels and do not draw any additional gates or wires. Complemented inputs are NOT available.**

Variables				Function
A	Z	D	G	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

 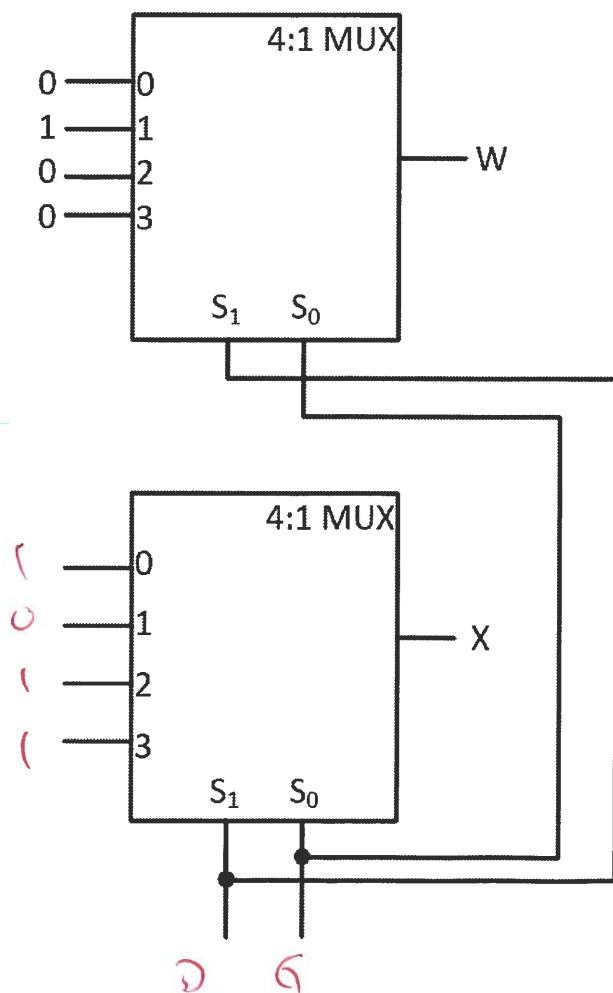

Extra copies of K-map for problem 2 (use as scratch copies, we will NOT grade them)

$E(A,B,C,D)$		AB			
		00	01	11	10
CD	00	1	1	0	1
	01	0	1	1	X
	11	0	X	X	0
	10	0	0	0	0

$E(A,B,C,D)$		AB			
		00	01	11	10
CD	00	1	1	0	1
	01	0	1	1	X
	11	0	X	X	0
	10	0	0	0	0

$E(A,B,C,D)$		AB			
		00	01	11	10
CD	00	1	1	0	1
	01	0	1	1	X
	11	0	X	X	0
	10	0	0	0	0

$E(A,B,C,D)$		AB			
		00	01	11	10
CD	00	1	1	0	1
	01	0	1	1	X
	11	0	X	X	0
	10	0	0	0	0

Extra copies of circuit for problem 4 (use as scratch copies, we will NOT grade them)

