

**ECE 120 Third Midterm Exam
Fall 2017**

Tuesday, November 28, 2017

Name: _____

SOLUTIONS

NetID: _____

Discussion Section and TA name:

11:00 AM	<input type="checkbox"/>	AD1 Ruby	<input type="checkbox"/>	AD8 Matt
12:00 PM	<input type="checkbox"/>	AD2 David	<input type="checkbox"/>	AD9 Matt
1:00 PM	<input type="checkbox"/>	AD3 David	<input type="checkbox"/>	ADA Yu-Hsuan
2:00 PM	<input type="checkbox"/>	AD4 Wanzheng	<input type="checkbox"/>	ADB Zhaoheng
3:00 PM	<input type="checkbox"/>	AD5 Wanzheng		
4:00 PM	<input type="checkbox"/>	AD6 Spencer	<input type="checkbox"/>	ADC Ruby
5:00 PM	<input type="checkbox"/>	AD7 Spencer	<input type="checkbox"/>	ADD Zhaoheng

- Be sure that your exam booklet has 9 pages.
- Write your name, netid and check discussion section on the title page.
- Do not tear the exam booklet apart, except for the last two pages.
- Use backs of pages for scratch work if needed.
- This is a closed book exam. You may not use a calculator.
- You are allowed one handwritten 8.5 x 11" sheet of notes (both sides).
- Absolutely no interaction between students is allowed.
- Clearly indicate any assumptions that you make.
- The questions are not weighted equally. Budget your time accordingly.
- Show your work.

Problem 1 19 points _____

Problem 2 12 points _____

Problem 3 23 points _____

Problem 4 24 points _____

Problem 5 22 points _____

Total 100 points _____

Problem 1 (19 points): FSM Design

In this problem you will implement an FSM that recognizes a **01** sequence. The circuit has one input x , one output z , and the output is 1 if and only if the pattern **01** has been detected in the input stream.


Example:

Input: $x = 0 \ 0 \ 1 \ 1 \ 1 \ 0 \ 1 \ 0 \ 1 \ 1 \ 1 \ 1 \ 0 \ 1 \ 1 \ 0 \ 1 \ . \ .$


Output: $z = 0 \ 0 \ 1 \ 0 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 0 \ 1 \ . \ .$

Note that the output sequence is delayed by 1 clock cycle compared to the input sequence because the output is a function of the flip-flop outputs.

 
1. (14 points) Draw the **Moore** state diagram and label the outputs and inputs. Give the meaning of each state. **To get full credit, use the minimum number of states.**



State	Meaning
"Start" 00	Pattern not yet seen
01	0 of pattern seen
10	01 of seen
11	Not used.

 

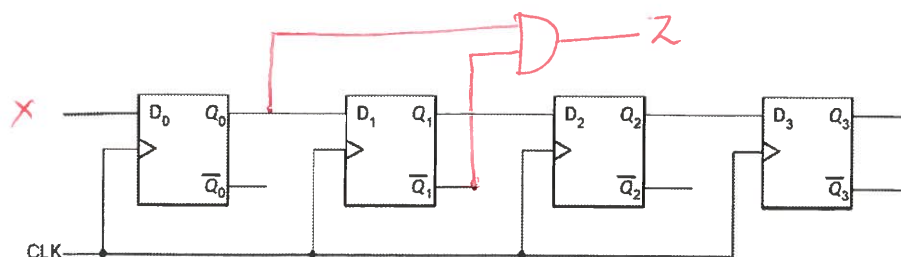
2. (5 points) Shown below is a 4-bit **shift register**, constructed with 4 positive-edge-triggered D flip-flops. Use this shift register and **only one gate** (NOT, AND, OR, NAND, NOR, XOR, or XNOR) to implement a circuit, which recognizes **01** just like the example at the top of the page. Be sure to label input x and output z .





Problem 2 (XX points): FSM Analysis

1. (4 points) Write the next state equation for S_1^+ from the FSM circuit given below.

$$S_1^+ = \underline{S_1 S_0 + S_0' M}$$

 

  
2. (8 points) Complete the state transition diagram (shown below) so that it corresponds to the FSM circuit above.



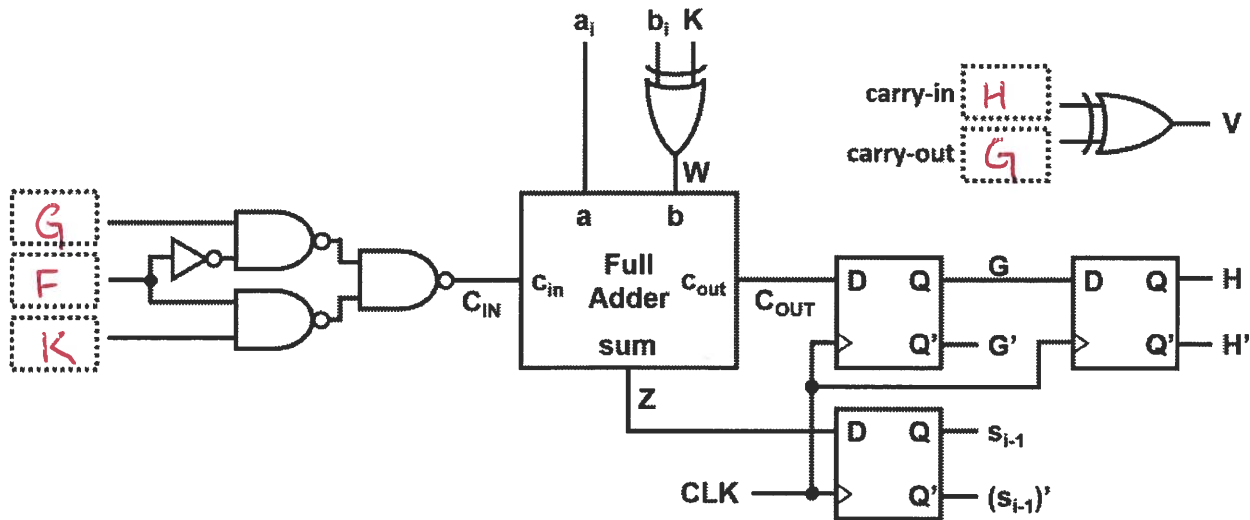Problem 3 (23 points): Serialized Design

The circuit below will be a serialized **n-bit 2's complement adder/subtractor circuit**. The inputs $a_{n-1}a_{n-2}\dots a_1a_0$ and $b_{n-1}b_{n-2}\dots b_1b_0$ are fed in serially (from LSB to MSB) and the output $s_{n-1}s_{n-2}\dots s_1s_0$ comes out serially (also from LSB to MSB). The control bit K determines whether addition or subtraction happens. Also available is a signal F that is 1 when a_0 and b_0 are input, and 0 otherwise. (F is not shown in the diagram, but you can use it.)

The output V will indicate that overflow has occurred, and is usually calculated as the XOR of the carry-in and the carry-out of the (a_{n-1}, b_{n-1}) calculation in the Full Adder. However, in this serialized design **V must depend only on the current state of the FSM.**



- (12 points) Complete the circuit above by writing the missing signals in the 5 boxes using 0, 1, F or any other signal labeled in the diagram. Complemented signals are **not** available, unless they are already shown in the diagram. You may **not** use additional wires or gates. Remember, the output V must depend only on the current state of the FSM.
- (4 points) When does V indicate whether overflow has occurred **compared to when s_{n-1} comes out of its flip-flop?** Circle the correct answer.

2 cycles earlier 1 cycle earlier same cycle 1 cycle later 2 cycles later

- (7 points) Setting $n=10$, calculate the costs of the following circuits using the component prices shown on the right.

Cost of the **serialized** 10-bit 2's complement adder/subtractor circuit with overflow detection (shown above):

81 cents


Cost of the corresponding **bit-sliced** 10-bit 2's complement adder/subtractor circuit with overflow detection:

104 cents

Component	Price (cents)
NOT	1
2-input NAND	2
2-input XOR	4
Full adder	6
Flip-flop	20

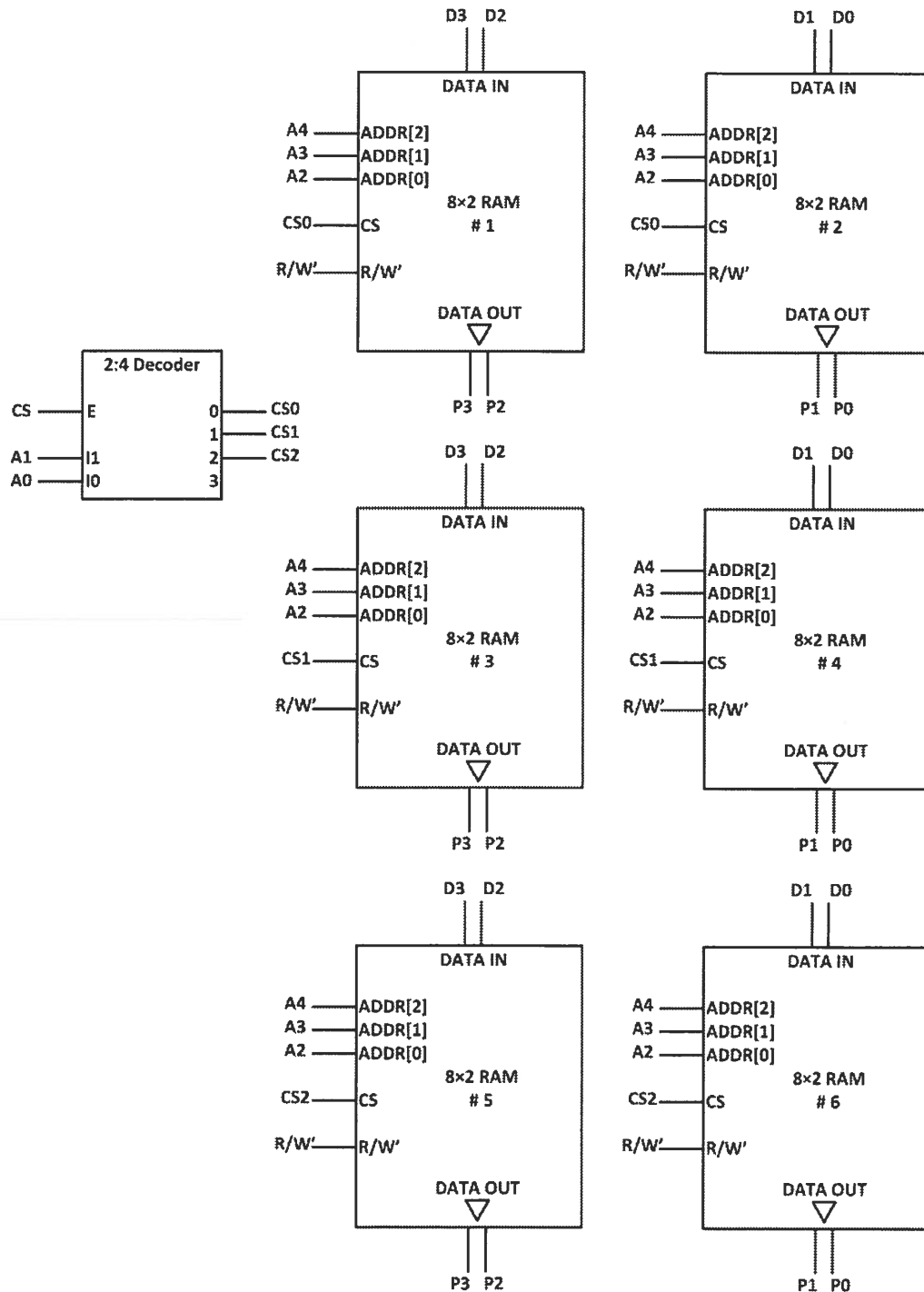Problem 4 (24 points): Memory

The ECE 120 instructors invited Doctor Strange to assist with the exam, and he obliged with the memory design presented below. Unfortunately for students, the instructors realized too late that he did not learn ECE 120 in this dimension, but in some other alternate dimension. Doctor Strange designed a **24×4 RAM**. His design, even though it works fine, is a bit... *strange*!



(The questions you need to answer are on the next page.)

Problem 4 (24 points): Memory (continued)

1. (12 points) A student attempts to write ($CS=1$ and $R/W'=0$) into the 24x4 RAM with data $D_3D_2D_1D_0 = 1011$ at address $A_4A_3A_2A_1A_0 = 01110$. Indicate in the table below which of the 8x2 RAMs are accessed by **circling YES or NO for each RAM**. If an 8x2 RAM is accessed, also write down the 2-bit Data-In and the 3-bit address ADDR[2:0] for that 8x2 RAM.

RAM #1 Accessed? YES / NO Data-In= _____ ADDR[2:0]= _____	RAM #2 Accessed? YES / NO Data-In= _____ ADDR[2:0]= _____
RAM #3 Accessed? YES / NO Data-In= _____ ADDR[2:0]= _____	RAM #4 Accessed? YES / NO Data-In= _____ ADDR[2:0]= _____
RAM #5 Accessed? YES / NO Data-In= 10 ADDR[2:0]= 011	RAM #6 Accessed? YES / NO Data-In= 11 ADDR[2:0]= 011

2. (12 points) Another student now attempts to write ($CS=1$ and $R/W'=0$) into the 24x4 RAM with data $D_3D_2D_1D_0 = 0100$ at address $A_4A_3A_2A_1A_0 = 01011$. Indicate in the table below which of the 8x2 RAMs are accessed by **circling YES or NO for each RAM**. If an 8x2 RAM is accessed, also write down the 2-bit Data-In and the 3-bit address ADDR[2:0] for that 8x2 RAM.

RAM #1 Accessed? YES / NO Data-In= _____ ADDR[2:0]= _____	RAM #2 Accessed? YES / NO Data-In= _____ ADDR[2:0]= _____
RAM #3 Accessed? YES / NO Data-In= _____ ADDR[2:0]= _____	RAM #4 Accessed? YES / NO Data-In= _____ ADDR[2:0]= _____
RAM #5 Accessed? YES / NO Data-In= _____ ADDR[2:0]= _____	RAM #6 Accessed? YES / NO Data-In= _____ ADDR[2:0]= _____

Problem 5 (22 points): LC-3 Interpretation and Assembly

The registers of an LC-3 processor currently have the values shown in the table to the right.

R0	x8888	R4	xCCCC	PC	x3710
R1	x9999	R5	xDDDD	IR	x993F
R2	xAAAA	R6	xEEEE	MAR	x370F
R3	xBBBB	R7	xFFFF	MDR	x993F

The table to the right shows some of the contents of the LC-3 processor's memory.

When the bits represent instructions, an interpretation has been provided for you in RTL.

Address	Contents	RTL Interpretation
x370F	1001 100 100 111111	R4 ← NOT(R4)
x3710	0101 101 000 000 001	R5 ← AND(R0,R1)
x3711	0000 100 000000001	BRn #1
x3712	0001 110 010 1 00001	R6 ← R2+#1
x3713	1010 111 0 1000 0001	R7 ← M[M[PC+x0081]]
...		...
x3793	0011 0111 1001 0100	(data: x3794)
x3794	0011 0111 1001 0110	(data: x3796)
x3795	0011 0111 1001 0011	(data: x3793)
x3796	0011 0111 1001 0101	(data: x3795)

Here is the question:

The LC-3 FSM **PROCESSES THREE INSTRUCTIONS**, starting with the fetch phase.

1. (7 points) Write a complete list of the sequence of values taken by the MAR register as the LC-3 processes these instructions. Use only as many lines as are necessary.

#1: x370F (initial value) #5: x3795
 #2: x3710 #6: x3793
 #3: x3711 #7: _____
 #4: x3713 #8: _____


2. (15 points) Complete the tables below with the **FINAL** values of each register and memory location (after processing the three instructions). **To receive credit, you must write your answers in hexadecimal.**

R4	xCCCC
R5	x8888
R6	xEEEE
R7	x3794

PC	x3714
IR	xAE81
MDR	x3794


LC-3 Instructions

LC-3 FSM

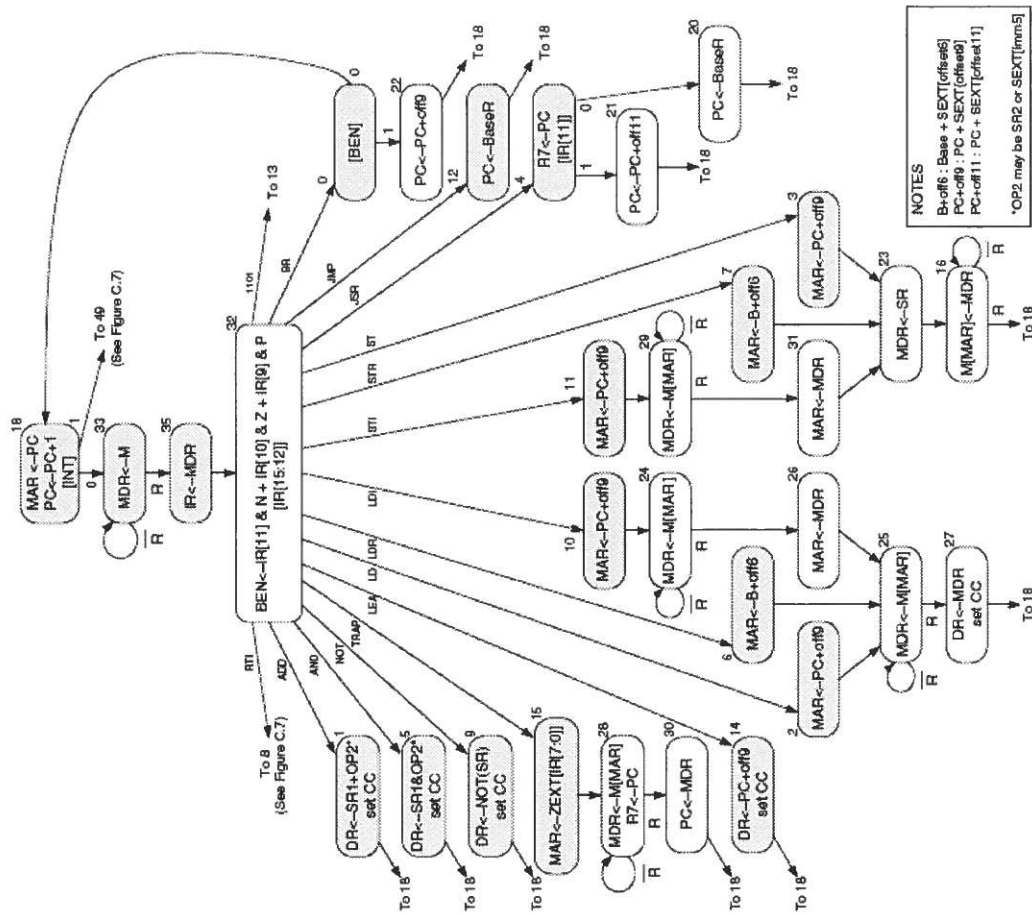

NOTES: RTL corresponds to execution (after fetch!); JSRR not shown

ADD	0001	DR	SR1	0	00	SR2	ADD DR, SR1, SR2	LD	0010	DR	PCOffset9		LD DR, PCOffset9		
							$DR \leftarrow SR1 + SR2, Setcc$								$DR \leftarrow M[PC + SEXT(PCOffset9)], Setcc$
ADD	0001	DR	SR1	1	imm5		ADD DR, SR1, imm5	LDI	1010	DR	PCOffset9		LDI DR, PCOffset9		
							$DR \leftarrow SR1 + SEXT(imm5), Setcc$								$DR \leftarrow M[M[PC + SEXT(PCOffset9)]], Setcc$
AND	0101	DR	SR1	0	00	SR2	AND DR, SR1, SR2	LDR	0110	DR	BaseR	offset6	LDR DR, BaseR, offset6		
							$DR \leftarrow SR1 \text{ AND } SR2, Setcc$								$DR \leftarrow M[BaseR + SEXT(offset6)], Setcc$
AND	0101	DR	SR1	1	imm5		AND DR, SR1, imm5	LEA	1110	DR	PCOffset9		LEA DR, PCOffset9		
							$DR \leftarrow SR1 \text{ AND } SEXT(imm5), Setcc$								$DR \leftarrow PC + SEXT(PCOffset9), Setcc$
BR	0000	n	z	p	PCOffset9		BR{nzp} PCOffset9	NOT	1001	DR	SR	111111	NOT DR, SR		
							((n AND N) OR (z AND Z) OR (p AND P)): $PC \leftarrow PC + SEXT(PCOffset9)$								$DR \leftarrow NOT SR, Setcc$
JMP	1100	000	BaseR	000000			JMP BaseR	ST	0011	SR	PCOffset9		ST SR, PCOffset9		
							$PC \leftarrow BaseR$								$M[PC + SEXT(PCOffset9)] \leftarrow SR$
JSR	0100	1	PCOffset11				JSR PCOffset11	STI	1011	SR	PCOffset9		STI SR, PCOffset9		
							$R7 \leftarrow PC, PC \leftarrow PC + SEXT(PCOffset11)$								$M[M[PC + SEXT(PCOffset9)]] \leftarrow SR$
TRAP	1111	0000	trapvect8				TRAP trapvect8	STR	0111	SR	BaseR	offset6	STR SR, BaseR, offset6		
							$R7 \leftarrow PC, PC \leftarrow M[ZEXT(trapvect8)]$								$M[BaseR + SEXT(offset6)] \leftarrow SR$

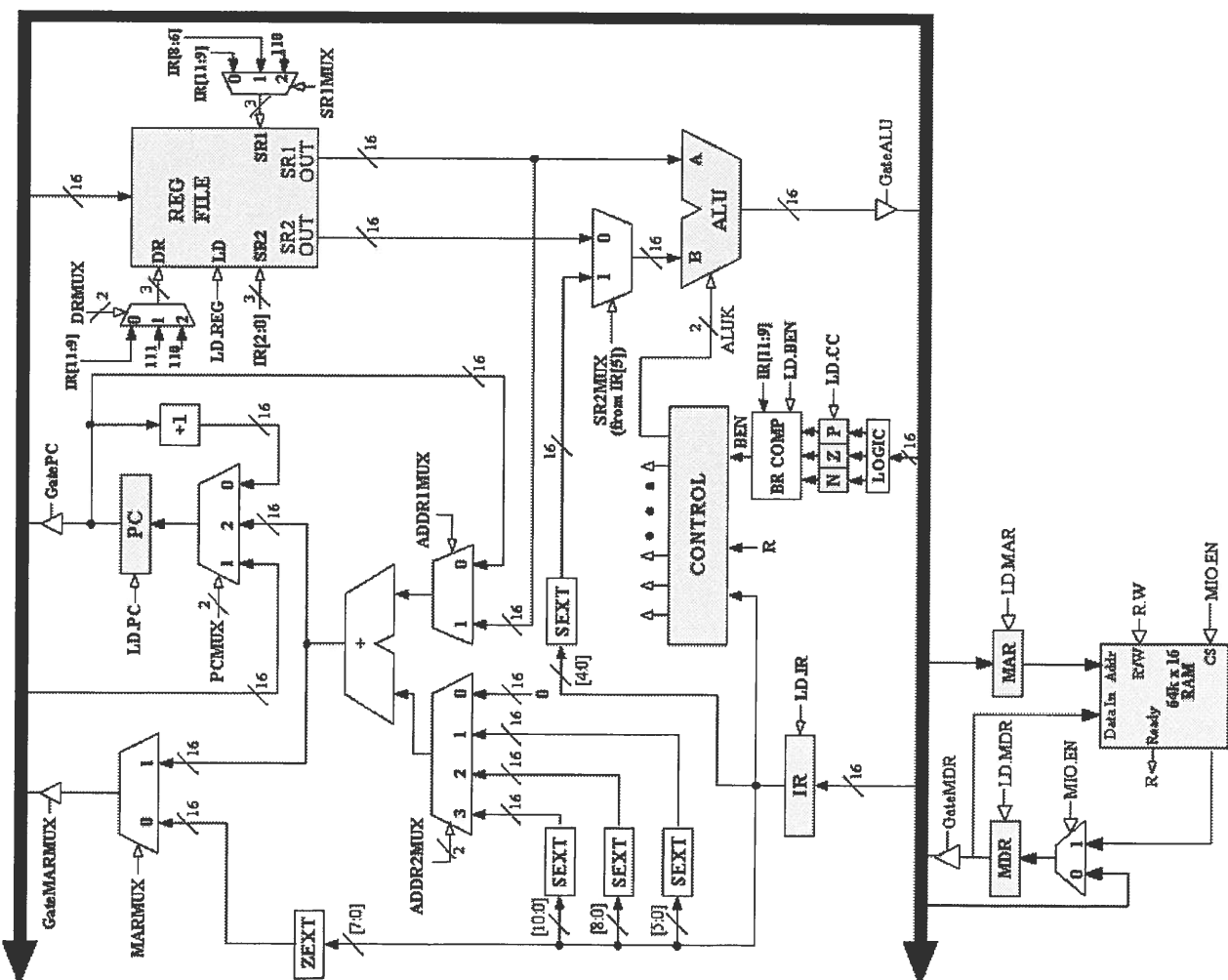

Signal	Description
LD.MAR	= 1, MAR is loaded
LD.MDR	= 1, MDR is loaded
LD.IR	= 1, IR is loaded
LD.PC	= 1, PC is loaded
LD.REG	= 1, register file is loaded
LD.BEN	= 1, updates Branch Enable (BEN) bit

Signal	Description
LD.CC	= 1, updates status bits from system bus
GateMARMUX	= 1, MARMUX output is put onto system bus
GateMDR	= 1, MDR contents are put onto system bus
GateALU	= 1, ALU output is put onto system bus
GatePC	= 1, PC contents are put onto system bus

MARMUX	$\begin{cases} = 0, \text{ chooses ZEXT IR[7:0]} \\ = 1, \text{ chooses address adder output} \end{cases}$
ADDR1MUX	$\begin{cases} = 0, \text{ chooses PC} \\ = 1, \text{ chooses reg file SR1 OUT} \end{cases}$
ADDR2MUX	$\begin{cases} = 00, \text{ chooses "0...00"} \\ = 01, \text{ chooses SEXT IR[5:0]} \\ = 10, \text{ chooses SEXT IR[8:0]} \\ = 11, \text{ chooses SEXT IR[10:0]} \end{cases}$
PCMUX	$\begin{cases} = 00, \text{ chooses PC} + 1 \\ = 01, \text{ chooses system bus} \\ = 10, \text{ chooses address adder output} \end{cases}$
SR1MUX	$\begin{cases} = 00, \text{ chooses IR[11:9]} \\ = 01, \text{ chooses IR[8:6]} \\ = 10, \text{ chooses "110"} \end{cases}$

MIO.EN	$\begin{cases} = 1, \text{ Enables memory,} \\ \text{ chooses memory output for MDR input} \\ = 0, \text{ Disables memory,} \\ \text{ chooses system bus for MDR input} \end{cases}$
R.W	$\begin{cases} = 1, \text{ M[MAR]<-MDR when MIO.EN = 1} \\ = 0, \text{ MDR<-M[MAR] when MIO.EN = 1} \end{cases}$
ALUK	$\begin{cases} = 00, \text{ ADD} \\ = 01, \text{ AND} \\ = 10, \text{ NOT A} \\ = 11, \text{ PASS A} \end{cases}$
DRMUX	$\begin{cases} = 00, \text{ chooses IR[11:9]} \\ = 01, \text{ chooses "111"} \\ = 10, \text{ chooses "110"} \end{cases}$