

**ECE 120 Third Midterm Exam
Spring 2017**

Tuesday, April 18, 2017

Name: _____

NetID: _____

Discussion Section and TA name:

9:00 AM	<input type="checkbox"/>	AB1 Rui	
10:00 AM	<input type="checkbox"/>	AB2 Rui	
11:00 AM	<input type="checkbox"/>	AB3 Matt	
12:00 PM	<input type="checkbox"/>	AB4 Pawel	
1:00 PM	<input type="checkbox"/>	AB5 Pawel	
2:00 PM	<input type="checkbox"/>	AB6 Gowthami	<input type="checkbox"/> ABA Hui ren
3:00 PM	<input type="checkbox"/>	AB7 Gowthami	<input type="checkbox"/> ABB Hui ren
4:00 PM	<input type="checkbox"/>	AB8 Yu-Hsuan	<input type="checkbox"/> ABC Sifan
5:00 PM	<input type="checkbox"/>	AB9 Yu-Hsuan	<input type="checkbox"/> ABD Surya

- **Be sure that your exam booklet has 9 pages.**
- **Write your name, netid and check discussion section on the title page.**
- **Do not tear the exam booklet apart, except for the last two pages.**
- **Use backs of pages for scratch work if needed.**
- **This is a closed book exam. You may not use a calculator.**
- **You are allowed one handwritten 8.5 x 11" sheet of notes (both sides).**
- **Absolutely no interaction between students is allowed.**
- **Clearly indicate any assumptions that you make.**
- **The questions are not weighted equally. Budget your time accordingly.**
- **Show your work.**

Problem 1 16 points _____

Problem 2 16 points _____

Problem 3 22 points _____


Problem 4 27 points _____

Problem 5 19 points _____


Total 100 points _____

 Problem 1 (16 points): Counter Design

The FSM drawn below consists of a 2-bit binary counter (S_1S_0 counts 0, 1, 2, 3, then returns to 0) and two inverters.



 1. (8 points) Draw a state transition diagram for the FSM. Label each node with the state identifier S_1S_0 and the output Y_1Y_0 . Do not cross transition arcs.





2. (5 points) In **TEN OR FEWER** words, what does the FSM do? *Hint: Look at the output sequence.*

3. (3 points) In the design above, the counter is treated as a black box—in other words, only the outputs S_1 and S_0 are available. If instead you had access to all transistors in the 2-bit binary counter design (that produces S_1S_0), what is the minimum number of additional transistors needed to implement the FSM that produces Y_1Y_0 ?

Minimum number of additional transistors = _____

  Problem 2 (16 points): Sequence Recognizer

Consider the state transition diagram shown below. Nodes are labeled with the state $S_2S_1S_0$ and the output R . Transition arcs are labeled with input B . **Assume that the FSM starts in state $S_2S_1S_0=000$.**




	S_0B			
	00	01	11	10
S_0^+				
00				
01				
11				
10				

- (8 points)** Fill in the K-map to the right for the next state bit S_0^+ as a function of the current state $S_2S_1S_0$ and the input B .
- (8 points)** The above FSM implements a sequence recognizer for non-overlapping instances of the sequence 10101. For example, if the FSM receives the input sequence 1010101, it produces the output sequence 0000100.

The figure to the right is the same as the one above, except that the two transitions coming from state 100 have been removed.

 Draw and label the transitions from state 100 so that the resulting FSM recognizes overlapping instances of the sequence 10101. That is, if the FSM receives the input sequence 1010101, it produces the output sequence 0000101.



Problem 3 (22 points): Memory


1. (10 points) The figure below shows the block diagram of a 4k x 8-bit RAM chip. Recall that 1k = 1024. Provide inputs to the RAM in order to store the **decimal value -6 in location (decimal) 30**. Answer in **binary** with the correct number of bits.

DATA _____


ADDR _____

CS _____

R / \overline{W} _____

 


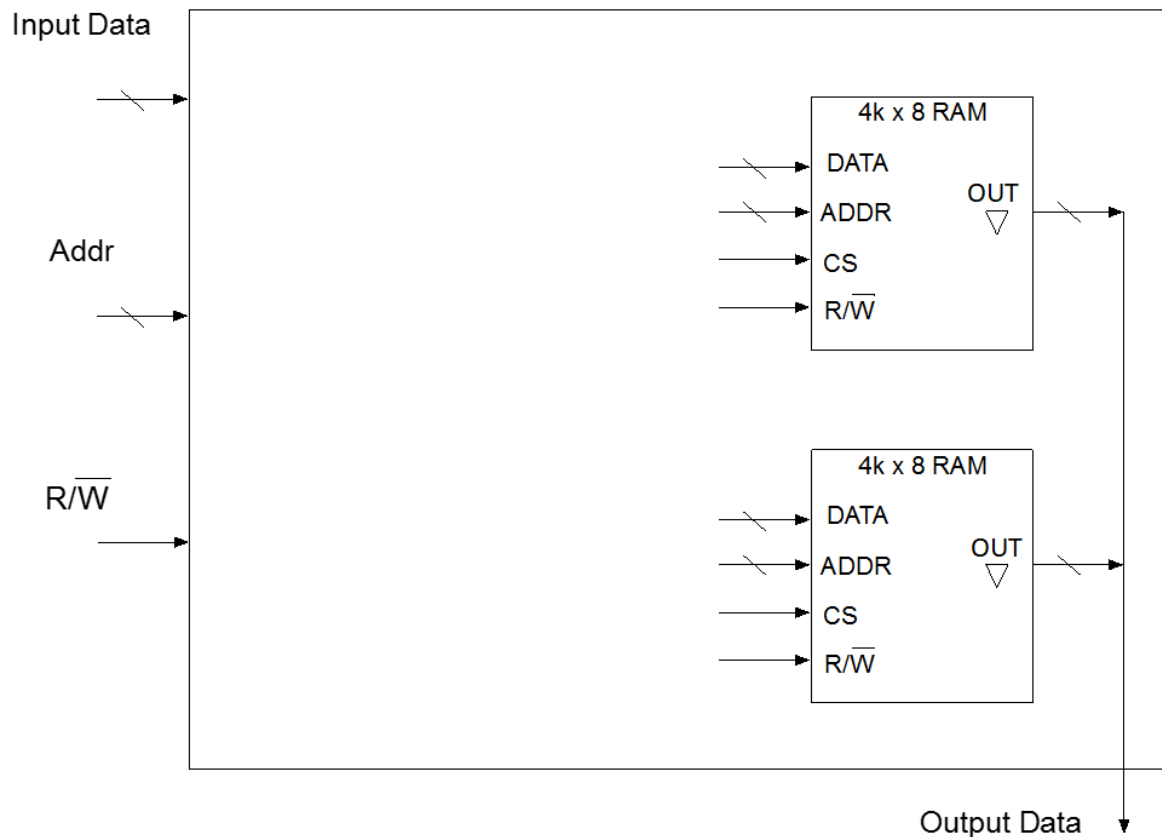2. (12 points) Use two of these 4k x 8-bit RAM chips (with CS) to build an 8k x 8-bit RAM (without CS). **Draw wires** to complete the logic below. The Output Data lines have been drawn for you. You may use **at most one additional gate** (AND, OR, or NOT). Label wires as needed (for example, Addr[3:0]) and write the number of wires wherever a “slash” is drawn.



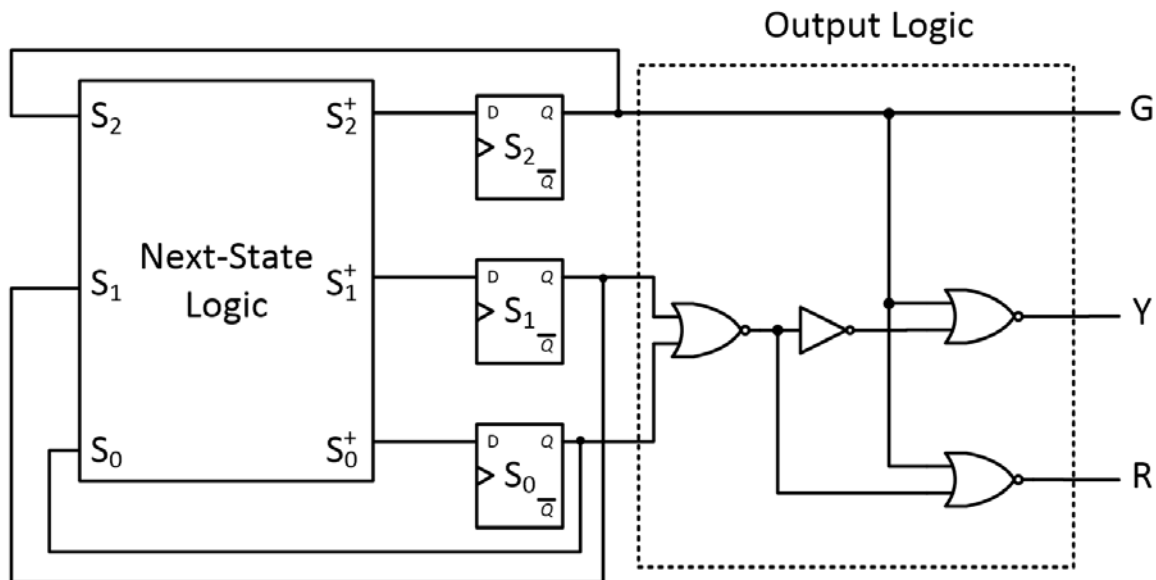Problem 4 (27 points): FSM Design

The city of Urbana has the following traffic light controller:



The next-state logic guarantees that the **FSM is a 3-bit binary up-counter** ($S_2S_1S_0$ counts the sequence 0, 1, 2, ..., 7, 0, 1, 2, ...), while the output logic translates the current state $S_2S_1S_0$ into outputs for the three lights: G (green), Y (yellow), and R (red).

The mayor of Urbana has requested the help of the ECE Department to extend the design to cope with emergency vehicles (fire engines, ambulances, police, and so forth.) Since the ECE 120 instructors are *very* busy, and the timing for midterm 3 was just perfect, your task is to extend the FSM as follows:

1. When an emergency vehicle nears the traffic light, your extended FSM receives a new input **E=1** (otherwise, input $E=0$).
 - a) If the **red light is lit ($R=1$)**, the FSM should **hold its current state** until E returns to 0 (after the emergency vehicle has passed).
 - b) If the **yellow light is lit ($Y=1$)**, the FSM should **continue to advance** in the same way as in the original design.
 - c) If the **green light is lit ($G=1$)**, the extended FSM must **light the yellow light ($Y=1$)** in the next cycle. (Safety is of utmost concern to the mayor. We don't want vehicles to suddenly stop and crash!)
2. If no emergency vehicle is present (**E=0**), the extended design should **continue to advance** in the same way as the original design behaved.

(The questions you need to answer are on the next page.)


Problem 4 (27 points): FSM Design, continued

1. (18 points) Write the state transition table for the extended design.

Current State			Input	Next State			Outputs		
S_2	S_1	S_0	E	S_2^+	S_1^+	S_0^+	G	Y	R
0	0	0	0						
0	0	1	0						
0	1	0	0						
0	1	1	0						
1	0	0	0						
1	0	1	0						
1	1	0	0						
1	1	1	0						
0	0	0	1						
0	0	1	1						
0	1	0	1						
0	1	1	1						
1	0	0	1						
1	0	1	1						
1	1	0	1						
1	1	1	1						

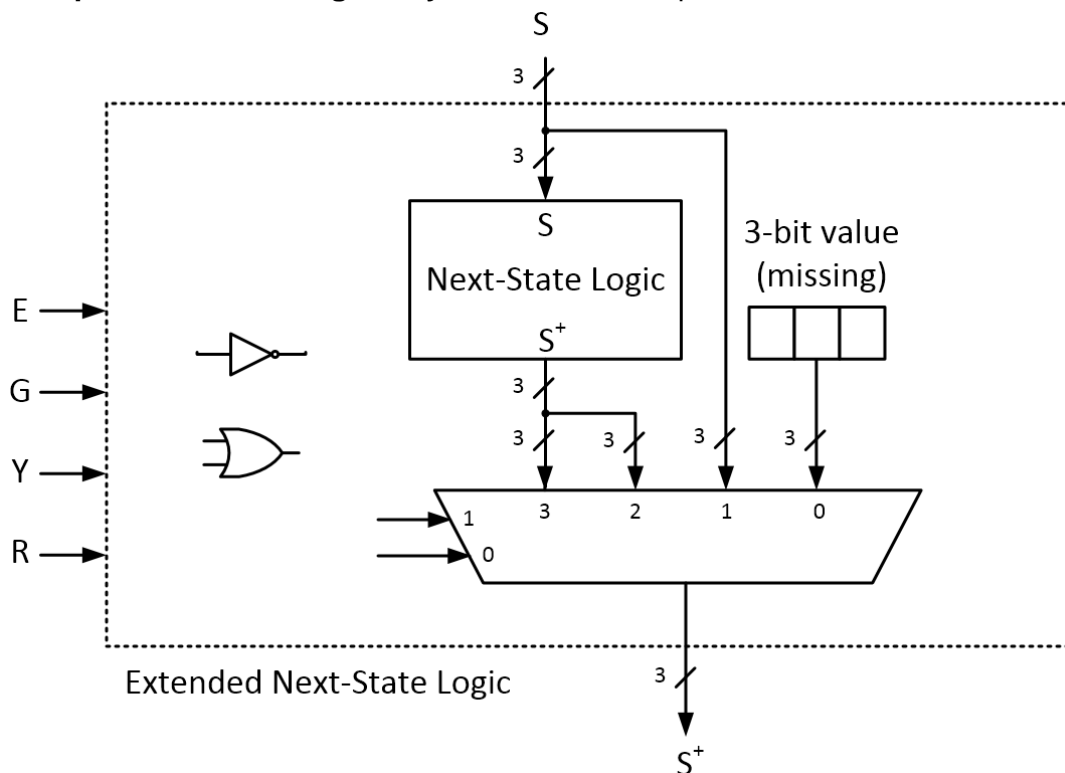2. (9 points) The circuit below extends the next-state logic as specified in the previous page to cope with the new input E, but it has not been finished yet.

- Write the missing 3-bit value in the provided boxes.
- Finish the design by drawing the missing wires. **You are NOT allowed to add any other component to the design, only wires.** Inverted inputs are not available.



Problem 5 (19 points): LC-3 Interpretation and Assembly

The registers of an LC-3 processor currently have the values shown in the table to the right.

R0	x0000	R4	x4444	PC	x4401
R1	x1111	R5	x5555	IR	x11E1
R2	x2222	R6	x6666	MAR	x4400
R3	x3333	R7	xFFFF	MDR	x11E1

The table to the right shows some of the contents of the LC-3 processor's memory.

When the bits represent instructions, an interpretation has been provided for you in RTL.

address	contents	RTL interpretation
x4400	0001 000 111 1 00001	$R0 \leftarrow R7+1$
x4401	1001 101 111 111111	$R5 \leftarrow \text{NOT}(R7)$
x4402	0110 110 100 000001	$R6 \leftarrow M[R4+1]$
x4403	1011 111 001000000	$M[M[PC+x040]] \leftarrow R7$

x4443	0100 0100 0100 0101	(data: x4445)
x4444	0100 0100 0100 0110	(data: x4446)
x4445	1111 1110 1110 1101	(data: xFEED)
x4446	1110 1100 1110 1011	(data: xECEB)

Here's the question:

The LC-3 FSM **PROCESSES THREE INSTRUCTIONS**, starting with the fetch phase.

1. (7 points) Write a complete list of the sequence of values taken by the MAR register as the LC-3 processes these instructions. Use only as many lines as are necessary.

#1: x4400 (initial value) #5: _____
 #2: _____ #6: _____
 #3: _____ #7: _____
 #4: _____ #8: _____


2. (12 points) Complete the tables below with the **FINAL** values (after processing of three instructions) of each register and memory location. **To receive credit, you must write your answers in hexadecimal.**

			memory address	contents
R5		PC	x4443	
R6		IR	x4444	
R7		MDR	x4445	
			x4446	

LC-3 Instructions


ADD	0001	DR	SR1	0	00	SR2	ADD DR, SR1, SR2	LD	0010	DR		PCoffset9	LD DR, PCoffset9
	DR ← SR1 + SR2, Setcc												DR ← M[PC + SEXT(PCoffset9)], Setcc
ADD	0001	DR	SR1	1		imm5	ADD DR, SR1, imm5	LDI	1010	DR		PCoffset9	LDI DR, PCoffset9
	DR ← SR1 + SEXT(imm5), Setcc												DR ← M[M[PC + SEXT(PCoffset9)]], Setcc
AND	0101	DR	SR1	0	00	SR2	AND DR, SR1, SR2	LDR	0110	DR	BaseR	offset6	LDR DR, BaseR, offset6
	DR ← SR1 AND SR2, Setcc												DR ← M[BaseR + SEXT(offset6)], Setcc
AND	0101	DR	SR1	1		imm5	AND DR, SR1, imm5	LEA	1110	DR		PCoffset9	LEA DR, PCoffset9
	DR ← SR1 AND SEXT(imm5), Setcc												DR ← PC + SEXT(PCoffset9), Setcc
BR	0000	n	z	p		PCoffset9	BR(nzp) PCoffset9	NOT	1001	DR	SR	111111	NOT DR, SR
	(n AND N) OR (z AND Z) OR (p AND P): PC ← PC + SEXT(PCoffset9)												DR ← NOT SR, Setcc
JMP	1100	000	BaseR			000000	JMP BaseR	ST	0011	SR		PCoffset9	ST SR, PCoffset9
	PC ← BaseR												M[PC + SEXT(PCoffset9)] ← SR
JSR	0100	1				PCoffset11	JSR PCoffset11	STI	1011	SR		PCoffset9	STI SR, PCoffset9
	R7 ← PC, PC ← PC + SEXT(PCoffset11)												M[M[PC + SEXT(PCoffset9)]] ← SR
TRAP	1111					trapvec8	TRAP trapvec8	STR	0111	SR	BaseR	offset6	STR SR, BaseR, offset6
	R7 ← PC, PC ← M[ZEXT(trapvec8)]												M[BaseR + SEXT(offset6)] ← SR

LC-3 FSM

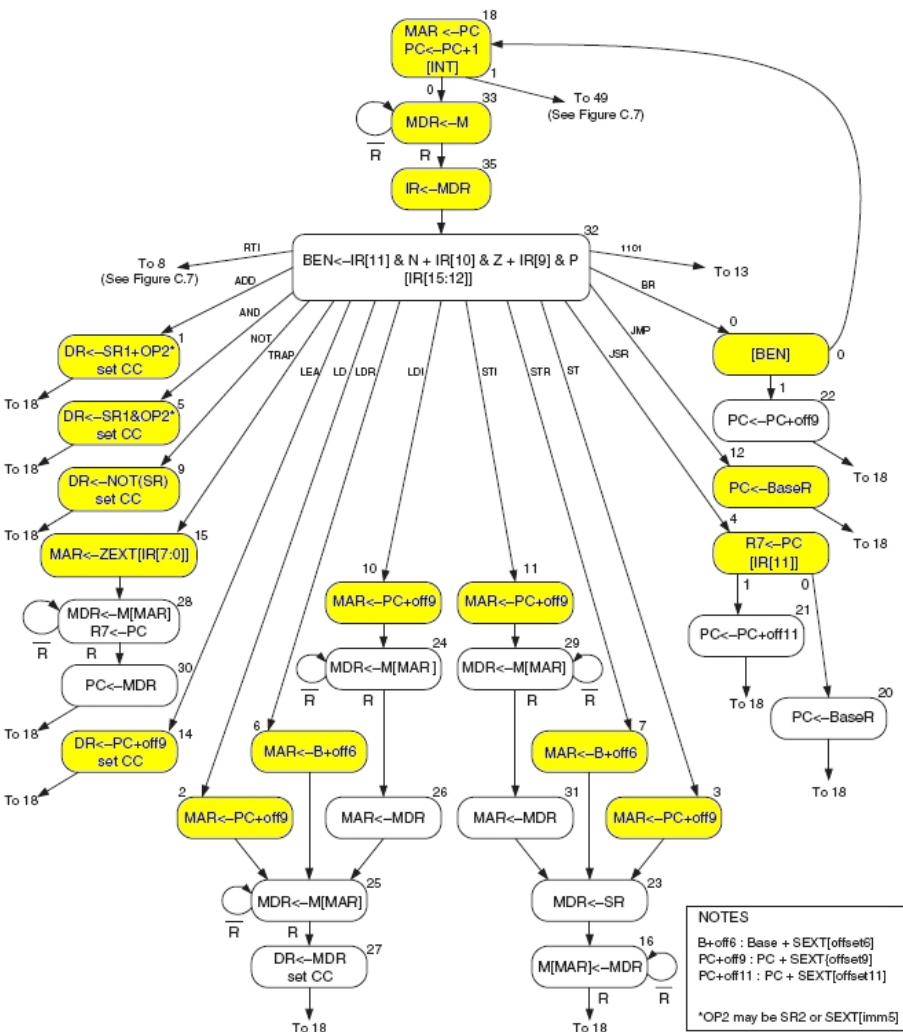

NOTES: RTL corresponds to execution (after fetch); JSRR not shown

LC-3 Datapath

 

LC-3 Datapath Control Signals

Signal	Description	Signal	Description
LD.MAR	= 1, MAR is loaded	LD.CC	= 1, updates status bits from system bus
LD.MDR	= 1, MDR is loaded	GateMARMUX	= 1, MARMUX output is put onto system bus
LD.IR	= 1, IR is loaded	GateMIO	= 1, MDR contents are put onto system bus
LD.PC	= 1, PC is loaded	GateALU	= 1, ALU output is put onto system bus
LD.REG	= 1, register file is loaded	GatePC	= 1, PC contents are put onto system bus
LD.BEN	= 1, updates Branch Enable (BEN) bit		
MARMUX	= 0, chooses ZEXT IR[7:0] = 1, chooses address adder output	MIO.EN	= 1, Enables memory, chooses memory output for MDR input = 0, Disables memory, chooses system bus for MDR input
ADDR1MUX	= 0, chooses PC = 1, chooses reg file SR1 OUT	R.W	= 1, M[MAR] < MDR when MIO.EN = 1 = 0, MDR < M[MAR] when MIO.EN = 1
ADDR2MUX	= 00, chooses "0...00" = 01, chooses SEXT IR[5:0] = 10, chooses SEXT IR[8:0] = 11, chooses SEXT IR[10:0]	ALUK	= 00, ADD = 01, AND = 10, NOT A = 11, PASS A
PCMUX	= 00, chooses PC + 1 = 01, chooses system bus = 10, chooses address adder output	DRMUX	= 00, chooses IR[11:9] = 01, chooses "111" = 10, chooses "110"
SR1MUX	= 00, chooses IR[11:9] = 01, chooses IR[8:6] = 10, chooses "110"		