

NAME _____

NETID _____

MIDTERM EXAM 2

(Closed book)

ECE 442

April 12, 2007

7:00 p.m. – 8:30 p.m.

Instructions: Write your name, and NetID where indicated. You are allowed to use one formula sheet ($8^{1/2} \times 11$) and a calculator. This examination consists of 4 problems. Each problem is worth 25 points. Show all work in order to receive partial credit.

Problem 1	Problem 2	Problem 3	Problem 4	Total

Formula Sheet

DIODE

$$I_D = I_S (e^{V_D/V_T} - 1), \text{ where } V_T = \frac{k_B T}{q} = 26 \text{ mV}$$

BIPOLAR (NPN forward active $I_B > 0$, $V_{CE} > V_{CE,sat}$)

$$I_C = I_S e^{V_{BE}/V_T} \cdot \left(1 + \frac{V_{CE}}{V_A}\right) \cong I_S e^{V_{BE}/V_T} \text{ where } V_T = \frac{k_B T}{q} = 26 \text{ mV}$$

$$I_C = \alpha I_E$$

$$I_C = \beta I_B \cdot \left(1 + \frac{V_{CE}}{V_A}\right) \cong \beta I_B$$

$$\alpha = \frac{\beta}{\beta + 1}$$


MOSFET (long channel model equations)

Define $V_{DSP} = V_{GS} - V_T$, where V_T is the threshold voltage

NMOS	PMOS
Triode Region (Linear) $V_{GS} > V_T$ & $V_{DS} < V_{DSP}$, $I_D = \frac{W}{L} \cdot k' \cdot \left((V_{GS} - V_T) \cdot V_{DS} - \frac{V_{DS}^2}{2} \right)$	Triode Region (Linear) $V_{GS} < V_T$ & $V_{DS} > V_{DSP}$, $I_D = \frac{W}{L} \cdot k' \cdot \left((V_{GS} - V_T) \cdot V_{DS} - \frac{V_{DS}^2}{2} \right)$
Active Region (Saturation) $V_{GS} > V_T$ & $V_{DS} \geq V_{DSP}$, $I_D = \frac{W}{L} \cdot \frac{k'}{2} \cdot (V_{GS} - V_T)^2 \cdot [1 + \lambda \cdot V_{DS}]$	Active Region (Saturation) $V_{GS} < V_T$ & $V_{DS} \leq V_{DSP}$, $I_D = \frac{W}{L} \cdot \frac{k'}{2} \cdot (V_{GS} - V_T)^2 \cdot [1 - \lambda \cdot V_{DS}]$
Body Effect $V_T = V_{To} + \gamma \cdot \left(\sqrt{ V_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right)$ $V_{GS} \leq V_T, I_D = 0$	Body Effect $V_T = V_{To} - \gamma \cdot \left(\sqrt{ V_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right)$ $V_{GS} \geq V_T, I_D = 0$

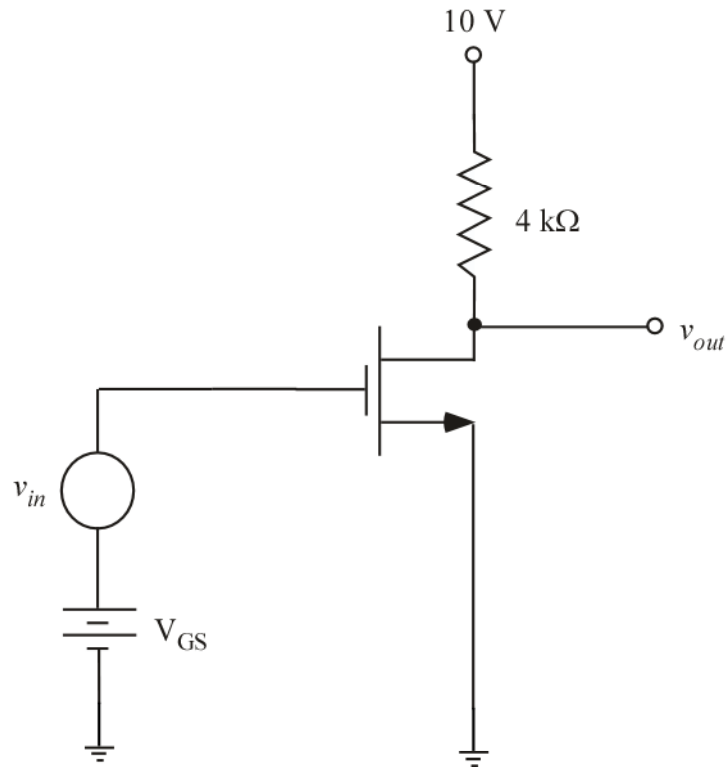PROBLEM 1 [25 points]

For the amplifier shown $\mu WC_{ox}/2L = 3 \text{ mA/V}^2$, $\lambda = 0.02/\text{V}$, and $V_T = 1.0 \text{ V}$.




- (a) Calculate V_{DSQ} when $V_{GSQ} = 1.5 \text{ V}$ (15 pts).

PROBLEM 1 (continued)

(b) Calculate the midband voltage gain for the stage (10 pts).

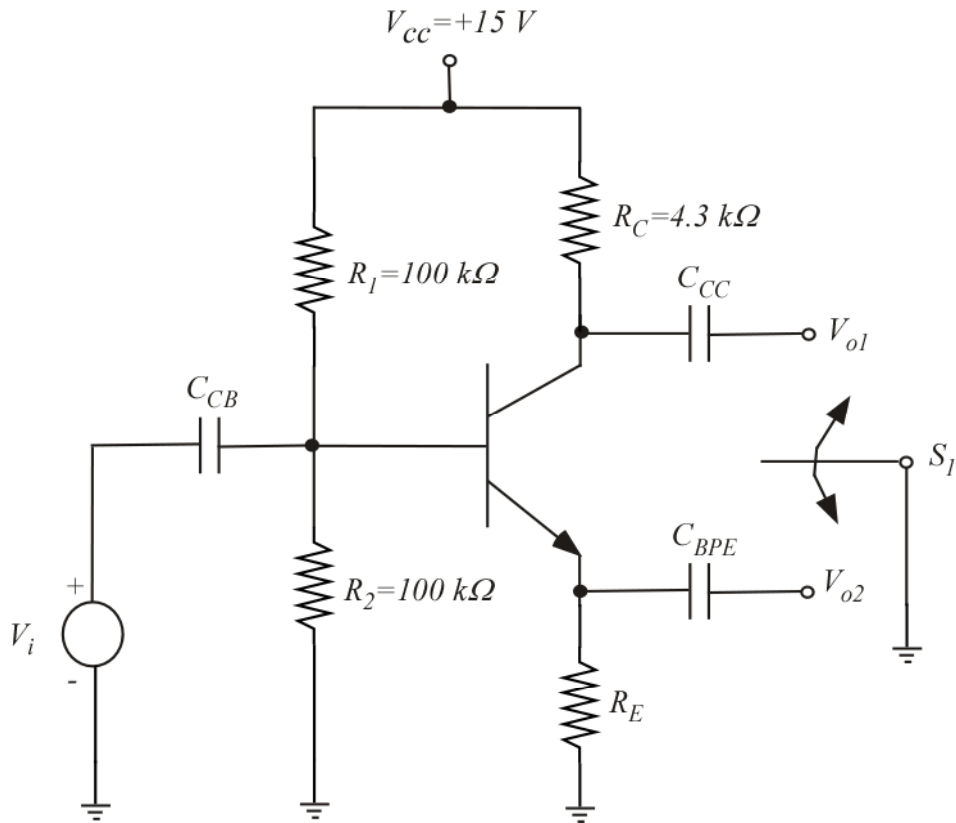PROBLEM 2 [25 points]

For the circuit shown, assume that β is very large. Also $C_\mu = 1$ pF and $\omega_T = 5$ GHz. It is desired to have a dc collector current of 1 mA. Use $V_{BEON} = 0.7$ V and assume that all coupling and bypass capacitors are midband short circuits.



(a) Determine the proper value for R_E

PROBLEM 2 (continued)

$$R_E = \underline{\hspace{2cm}}$$

- (b) The switch S_I is set in the off position (as shown in the figure) and the output is collected at V_{o1} . What is the midband voltage gain?

$$A_{MB} = \underline{\hspace{2cm}}$$

- (c) The switch S_I is now connected to V_{o1} and the output is collected at V_{o2} . What is the midband voltage gain?

$$A_{MB} = \underline{\hspace{2cm}}$$

PROBLEM 2 (continued)

- (d) Next, the switch S_I is connected to V_{o2} and the output is collected at V_{o1} . What is the midband voltage gain?


$$A_{MB} = \underline{\hspace{2cm}}$$

- (e) Determine the upper 3dB corner frequency for the common-emitter configuration of this amplifier.

$$f_{3dB} = \underline{\hspace{2cm}}$$

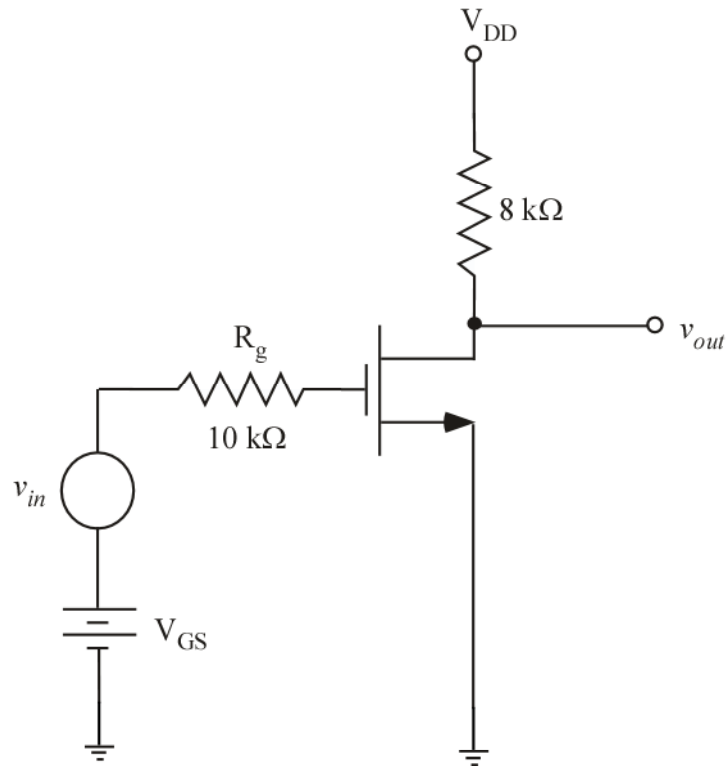PROBLEM 3 [25 points]

Consider the MOSFET circuit shown below, with $g_m=3 \text{ mA/V}$ and $r_{ds}=63 \text{ k}\Omega$. Assume that $C_{gs}=1 \text{ pF}$ and $C_{gd}=0.1 \text{ pF}$.



(a) Draw the midband equivalent circuit

PROBLEM 3 (continued)

(b) Calculate the midband voltage gain

(c) Draw the high-frequency equivalent circuit

PROBLEM 3 (continued)

(d) Calculate the upper corner frequency

(e) Calculate the unity current-gain frequency point f_T

PROBLEM 4 [25 points]

For the opamp circuit shown, determine the values of:

(a) $v_1 \Rightarrow v_I = 0$ since it is a virtual ground

(b) $i_1 \Rightarrow$

(c) $i_2 \Rightarrow$

(d) $v_o \Rightarrow$

(e) $i_L \Rightarrow$

(f) $i_o \Rightarrow$

