

NAME _____

MIDTERM EXAM SOLUTIONS

ECE 451

October 15, 2014

12:00 – 12:50 p.m.

Instructions: Write your name and section where indicated. Show all work. Indicate the units of your answers.

Mason's non-touching loop rule:

$$T = \frac{P_1 \left[1 - \sum L(1)^{(1)} + \sum L(2)^{(1)} - \dots \right] + P_2 \left[1 - \sum L(1)^{(2)} + \sum L(2)^{(2)} - \dots \right] + \dots}{1 - \sum L(1) + \sum L(2) - \sum L(3) + \dots}$$

Problem 1 (25 pts)	Problem 2 (25 pts)	Problem 2 (25 pts)	Problem 2 (25 pts)	Total (100 pts)

1. A transmission line of characteristic impedance Z_o , length d and propagation constant β is terminated with an open.

(a) Find the input impedance.

(b) Draw a rough sketch of Z_{in}/Z_o for βd ranging from 0 to π and label the frequency bands where the transmission line looks capacitive and where it looks inductive.


(c) At what frequencies does this open transmission line look like a short circuit?

(a) For a transmission line of length d , we have:

$$Z_{in} = Z_o \left\{ \frac{Z_L + jZ_o \tan \beta d}{Z_o + jZ_L \tan \beta d} \right\}$$

If $Z_L \rightarrow \infty$, then $Z_{in} = -jZ_o \cotan \beta d$

(b)

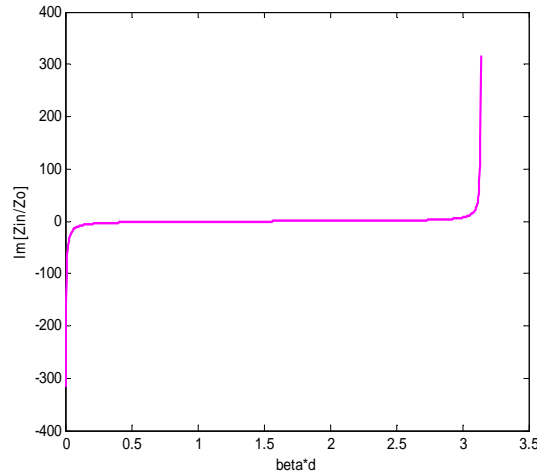


(c) The TL looks like a short for

$$\beta d = \frac{(2n+1)\pi}{2}, n = 0, 1, 2, \dots \text{ or } \frac{2\pi f d}{v} = \frac{(2n+1)\pi}{2}, n = 0, 1, 2, \dots$$

where v is the propagation velocity in the TL. This leads to: $f = \frac{(2n+1)v}{4d}, n = 0, 1, 2, \dots$

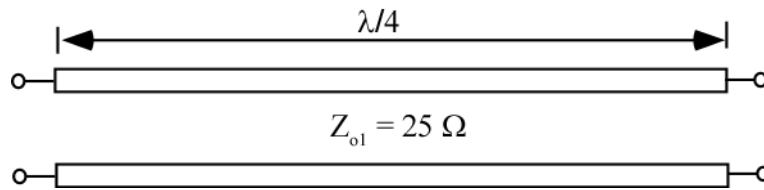2. For the transmission line shown below, write the scattering parameter matrix as measured on a 50-Ω network analyzer.



$$S_{11} = \frac{(1 - X^2)\Gamma}{1 - X^2\Gamma^2} \quad \text{and} \quad S_{21} = \frac{(1 - \Gamma^2)X}{1 - X^2\Gamma^2}$$

$$\text{with } \Gamma = \frac{Z_{o1} - Z_o}{Z_{o1} + Z_o} \quad \text{and} \quad X = e^{-j\frac{2\pi l}{\lambda}}$$

$$X = e^{-j\frac{2\pi \lambda}{\lambda} \frac{1}{4}} = e^{-j\frac{\pi}{2}} = -j$$


$$\Gamma = \frac{25 - 50}{25 + 50} = \frac{-25}{75} = -\frac{1}{3}$$

$$S_{11} = \frac{(1 - j^2)(-1/3)}{1 - (j^2)(1/9)} = \frac{(2)(-1/3)}{1 + 1/9} = \frac{(-2/3)}{10/9} = -3/5 = -0.6$$

$$S_{21} = \frac{(1 - 1/9)(-j)}{1 - (j^2)(1/9)} = \frac{(-j8/9)}{10/9} = -\frac{4j}{5} = -0.8j$$

$$S = \begin{bmatrix} -0.6 & -0.8j \\ -0.8j & -0.6 \end{bmatrix}$$

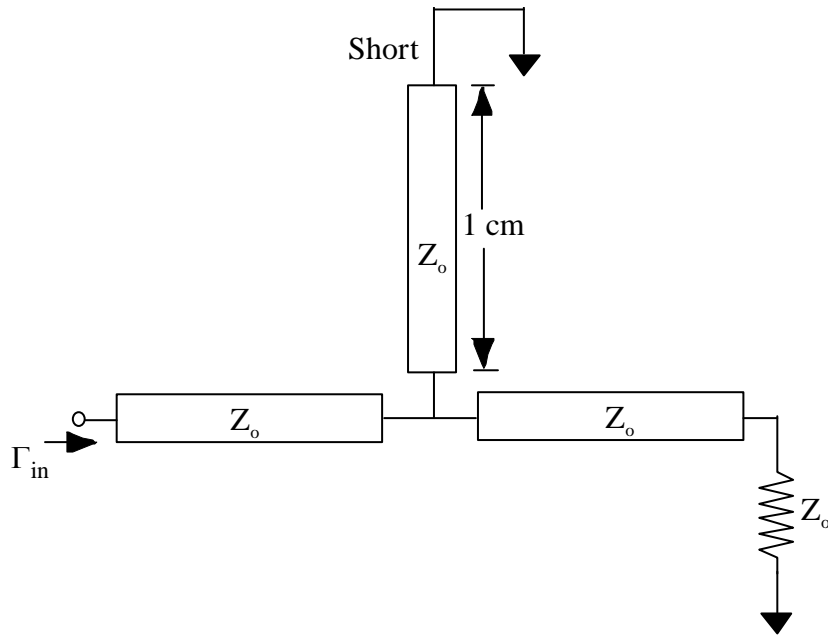3. For the circuit shown below (lab student unknown), the transmission lines use air as dielectric. What is the lowest frequency for which $\Gamma_{in} = 0$? (Use Z_o as your reference impedance).



Solution

$\Gamma_{in}=0$ when shorted stub length= $\lambda/4$, or

$$\lambda = \frac{c}{f} = 4cm$$

$$f = \frac{c}{\lambda} = \frac{0.3 \times 10^9}{4 \times 10^{-2}} = 7.5 \text{ GHz}$$

4. A lossless transmission line has the following per unit length parameters: $L = 80 \text{ nH}\cdot\text{m}^{-1}$, $C = 200 \text{ pF}\cdot\text{m}^{-1}$. Consider a traveling wave on the transmission line with a frequency of 1 GHz.

- (a) What is the attenuation constant?
- (b) What is the phase constant?
- (c) What is the phase velocity?
- (d) What is the characteristic impedance of the line?
- (e) Now consider that the dielectric is replaced by a dielectric with $\epsilon_r = 1$ (or air). The capacitance per unit length of the line is now $C(\text{air}) = 50 \text{ pF}\cdot\text{m}^{-1}$. What is the effective relative dielectric constant of the line?

(a) $\alpha = 0$

(b) $\beta = \omega\sqrt{LC} = 25.13 \text{ radians} / \text{m}$

(c) $v_p = \omega / \beta = \frac{1}{\sqrt{LC}} = 2.5 \times 10^8 \text{ m} / \text{s}$

(d) $Z_o = \sqrt{L / C} = 20 \Omega$

(e) $\epsilon_r = \frac{200}{50} = 4$